



Instructor: Anas Toma

| NAME | ID NUM | SEC |
|-----------------------------|----------|--------------|
| أحمد عبد الله جبر القرم - 1 | 11819195 | 3/8:00-11:00 |
| - | - | - |

Experiment 2: 4-bit Adder with Structural and Behavioral Implementation

Introduction :

In this experiment I will try to design an 4 Bit Adder using (vhdl) and Zboard from Xilinx

Step by step in tow part :

- 1- Structural Implementation: starting from half adder .
- 2- Behavioral Implementation : using IEEE library.

Tools used in Lap :

- 1- Computer lap.
- 2- Vivado software .
- 3- Zboard from Xilinx.
- 4- VHDL


Part 1 : Structural Implementation.

Procedure :

At first build the half adder that contain (XOR) and (AND) gate

$$S = A \oplus B \quad Cout = A.B$$

| A | B | S | Cout |
|---|---|---|------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

 


```
Project Summary x fa.vhd x bit4Adder.vhd x Adder.vhd * x
C:/Users/Ahmad/Desktop/A4BitAdder/A4BitAdder.srcs/sources_1/new/Adder.vhd

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity Adder is
4     port (a:in std_logic;
5           b:in std_logic;
6           s:out std_logic;
7           c:out std_logic
8         );
9 end Adder;
10 architecture arc of adder is
11 begin
12     s <= a xor b;
13     c <= a and b ;
14 end arc ;
15
16
```

Simulation for Half Adder:


Testbench code:

```
6
7 architecture Behavioral of hadders is
8 component adder port (a:in std_logic;b:in std_logic;s:out std_logic;c:out std_logic);
9 end component;
10 signal a:std_logic:='0';
11 signal b:std_logic:='0';
12 signal s:std_logic:='0';
13 signal c:std_logic:='0';
14 begin
15 uut : adder port map (a=>a,b=>b,s=>s,c=>c);
16 sim:process
17 begin
18
19     a<='0';
20     b<='0';
21     wait for 10 ns;
22
23     a<='1';
24     b<='0';
25     wait for 10 ns;
26
27     a<='0';
28     b<='1';
29     wait for 10 ns;
30
31     a<='1';
32     b<='1';
33     wait for 10 ns;
34 wait;
35 end process;
36 end Behavioral;
```

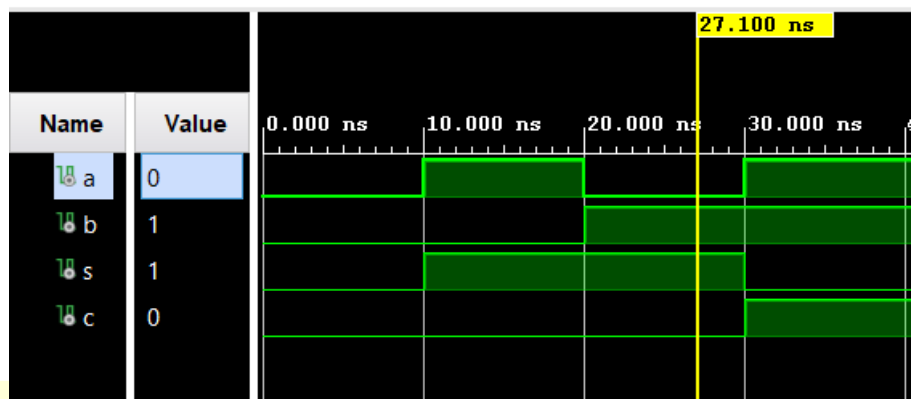

Then build Full Adder where Composed of 2 (Half Adder) and (OR) gate as shown :

| A | B | Cin | S | Cout |
|---|---|-----|---|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

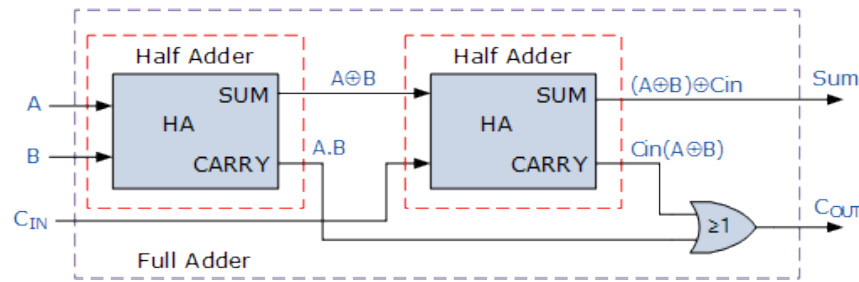

```

Project Summary x fa.vhd * x bit4Adder.vhd x Adder.vhd * x
C:/Users/Ahmad/Desktop/A4BitAdder/A4BitAdder.srcs/sources_1/new/fa.vhd

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity fa is
4     Port ( a : in STD_LOGIC;
5           b : in STD_LOGIC;
6           cin : in STD_LOGIC;
7           s : out STD_LOGIC;
8           cout : out STD_LOGIC);
9 end fa;
10 architecture Behavioral of fa is
11     component adder port (a,b:in std_logic;s,c:out std_logic);
12 end component;
13
14     signal w_sum,w_cry1,w_cry2:std_logic;
15
16     begin
17
18     mod1: adder port map (
19         a=>a,
20         b=>b,
21         s=>w_sum,
22         c=>w_cry1
23     );
24     mod2: adder port map (
25         a=>w_sum,
26         b=>cin,
27         s=>s,
28         c=>w_cry2
29     );
30     cout<= w_cry1 or w_cry2;
31 end Behavioral;
32


```

Simulation and testbench code :


```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity fas is
4     -- Port ( );
5 end fas;
6 architecture Behavioral of fas is
7
8     component fa port (a,b,cin:in std_logic;s,cout:out std_logic);
9 end component;
10
11     signal a,b,cin,s,cout:std_logic:='0';
12
13     begin
14
15     uut: fa port map (
16         a=>a,
17         b=>b,
18         cin=>cin,
19         cout=>cout,
20         s=>s
21     );
22
23     sim:process
24     begin
25
26         a<='0';
27         b<='0';
28         cin<='0';
29         wait for 10 ns;
30
31         a<='1';
32         b<='0';
33         cin<='0';
34         wait for 10 ns;
35
36         a<='1';
37         b<='1';
38         cin<='0';
39         wait for 10 ns;
40
41         a<='0';
42         b<='1';
43         cin<='1';
44         wait for 10 ns;
45
46         a<='1';
47         b<='1';
48         cin<='1';
49         wait for 10 ns;
50
51         a<='0';
52         b<='1';
53         cin<='1';
54         wait for 10 ns;
55
56         a<='1';
57         b<='1';
58         cin<='1';
59         wait for 10 ns;
60
61         wait;
62     end process;
63

```

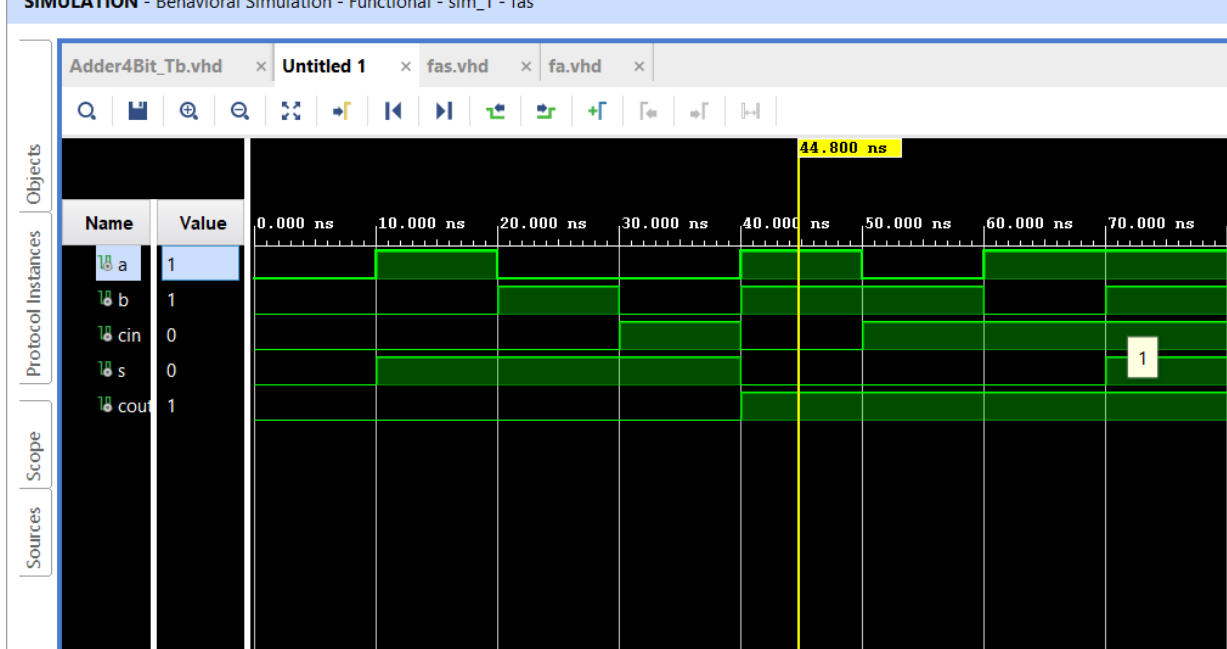

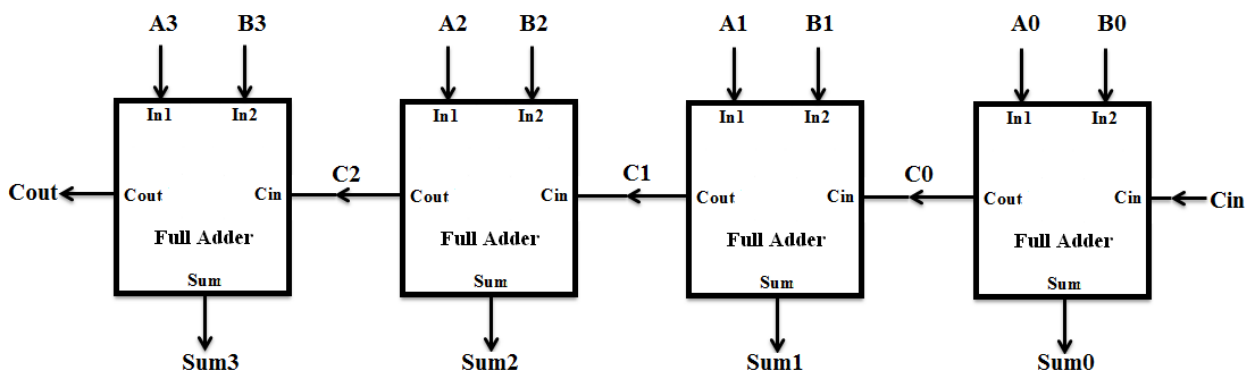After that i used 4 Full Adder to build the 4 bit Adder



```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity bit4Adder is
5      Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
6            B : in STD_LOGIC_VECTOR (3 downto 0);
7            S : out STD_LOGIC_VECTOR (3 downto 0);
8            Cout : out STD_LOGIC);
9  end bit4Adder;
10 architecture Behavioral of bit4Adder is
11     component Adder port (
12         a:in std_logic;
13         b:in std_logic;
14         cin:in std_logic;
15         s:out std_logic;
16         cout:out std_logic
17     );
18 end component;
19 signal c1,c2,c3,c4:std_logic;
20 begin
21     mod1:Adder port map(
22         a=>A(0),
23         b=>B(0),
24         cin=>'0',
25         s=>S(0),
26         cout=>c1
27     );
28
29     mod2:Adder port map(
30         a=>A(1),
31         b=>B(1),
32         cin=>c1,
33         s=>S(1),
34         cout=>c2
35     );
36
37     mod3:Adder port map(
38         a=>A(2),
39         b=>B(2),
40         cin=>c2,
41         s=>S(2),
42         cout=>c3
43     );
44
45     mod4:Adder port map(
46         a=>A(3),
47         b=>B(3),
48         cin=>c3,
49         s=>S(3),
50         cout=>c4
51     );
52 end Behavioral;

```

Synthesis, Implementation, and Bitstream Generation thin program the Zboard and I had checked the circuit .

| Inputs | Package Pin | I/O Std |
|----------------|--------------------|----------------|
| SW0 | F22 | LVC MOS18 |
| SW1 | G22 | LVC MOS18 |
| SW2 | H22 | LVC MOS18 |
| SW3 | F21 | LVC MOS18 |
| SW4 | H19 | LVC MOS18 |
| SW5 | H18 | LVC MOS18 |
| SW6 | H17 | LVC MOS18 |
| SW7 | M15 | LVC MOS18 |
| Outputs | Package Pin | I/O Std |
| LD0 | T22 | LVC MOS33 |
| LD1 | T21 | LVC MOS33 |
| LD2 | U22 | LVC MOS33 |
| LD3 | U21 | LVC MOS33 |
| LD4 | V22 | LVC MOS33 |

Write Behavioral code in vivado as shown :


```
A4BitAdderB.vhd x A4BitAdder_TB.vhd x Untitled 4 x
E:/projects/4BitAdderB/4BitAdderB.srcs/sources_1/new/A4BitAdderB.vhd

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.std_logic_unsigned.ALL ;
4  use IEEE.numeric_std.ALL;
5  entity A4BitAdderB is
6      Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
7            B : in STD_LOGIC_VECTOR (3 downto 0);
8            S : out STD_LOGIC_VECTOR (3 downto 0);
9            Cout : out STD_LOGIC);
10 end A4BitAdderB;
11
12 architecture Behavioral of A4BitAdderB is
13     signal sum:std_logic_vector(4 downto 0);
14     begin
15         sum <= ('0'&A)+('0'&B);
16         S(0)<=sum(0);
17         S(1)<=sum(1);
18         S(2)<=sum(2);
19         S(3)<=sum(3);
20         Cout<=sum(4);
21     end Behavioral;
22
```

Simulation :

There is the testbench code :

```
9  architecture Behavioral of A4BitAdder_TB is
10  component A4BitAdderB port (
11      A:in std_logic_vector;
12      B:in std_logic_vector;
13      S:out std_logic_vector;
14      Cout:out std_logic
15  );
16  end component;
17  signal A,B,S:std_logic_vector (3 downto 0):="0000";
18  signal Cout:std_logic:='0';
19
20  begin
21      uut : A4BitAdderB port map (
22          A=>A,
23          B=>B,
24          S=>S,
25          Cout=>Cout
26      );
27      sim : process
28      begin
29          for i in 1 to 16 loop
30              for i in 1 to 16 loop
31                  A<=A+'1';
32                  wait for 10 ns;
33              end loop;
34              B<=B+'1';
35              wait for 10 ns;
36          end loop;
37      end process;
38  end Behavioral;
```

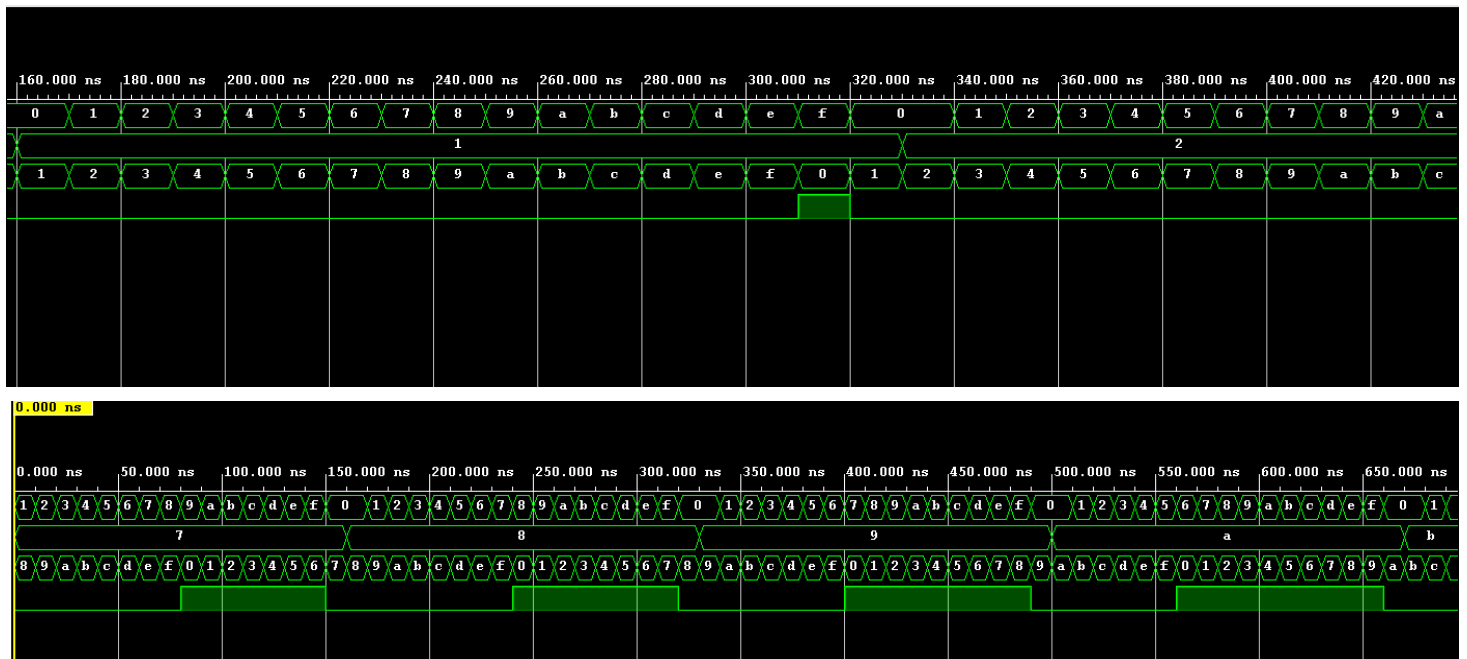

After Simulate my design . i used the same constraint file from part1

Run the Synthesis, Implementation, and Bitstream Generation processes

Use the Hardware Manger to program your FPGA.

Use the switches and notice the LEDs to verify that your circuit functions correctly.

Conclusion:

In this experiment i learned that i can use switches on the kit as a binary input by specifying in the (.XDC) file. In the same file we can specify the LEDs to show the binary output of our operations.

I got familiar with Zboard kit and i implemented a simple 4BitAdder circuit using VHDL. This helped me learn about the design, simulation and synthesizing processes.