



Instructor: Anas Toma

NAME	ID NUM	SEC
أحمد عبد الله جبر القرم 1-	11819195	3/8:00-11:00
-	-	-

Experiment 3:

Part 1 : Asynchronous Ripple Counter.

Tools used in Lap :

- 1- Computer lap.
- 2- Vivado software .
- 3- Zboard from Xilinx.
- 4- VHDL


Introduction :

In this part, I will try to build a 4-bit Asynchronous ripple counter using T flip-flops.

1- T Flip-Flop

Implementation for T flip-flop with following pins:

 - a. **T** : Synchronous Input (0: No change , 1: Toggle)
- b. **CLK**: positive edge trigger clock.
- c. **Clear**: Asynchronous active low clear.
- d. **Q** : output.
- e. **QBAR** : output .




T	Q	Q'
0	0	0
1	0	1
0	1	0
1	1	0

T Flip-Flop VHDL CODE :

```
Project Summary x TFF.vhd x
E:/projects/EX3_4BRC_Part1/EX3_4BRC.srscs/sources_1/new/TFF.vhd

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity TFF is
4     Port ( T : in STD_LOGIC;
5           CLK : in STD_LOGIC;
6           Clear : in STD_LOGIC;
7           Q : out STD_LOGIC;
8           Qbar : out STD_LOGIC);
9 end TFF;
10 architecture Behavioral of TFF is
11     signal temp : std_logic := '0';
12 begin
13     process (CLK,Clear)
14     begin
15         if Clear='0'then
16             temp<='0';
17         elsif (CLK'event and CLK='1' and T='1') then
18             temp<=not temp;
19         end if;
20     end process;
21     Q <= temp;
22     Qbar <= not temp;
23 end Behavioral;
24
```

Simulation for T Flip-Flop:

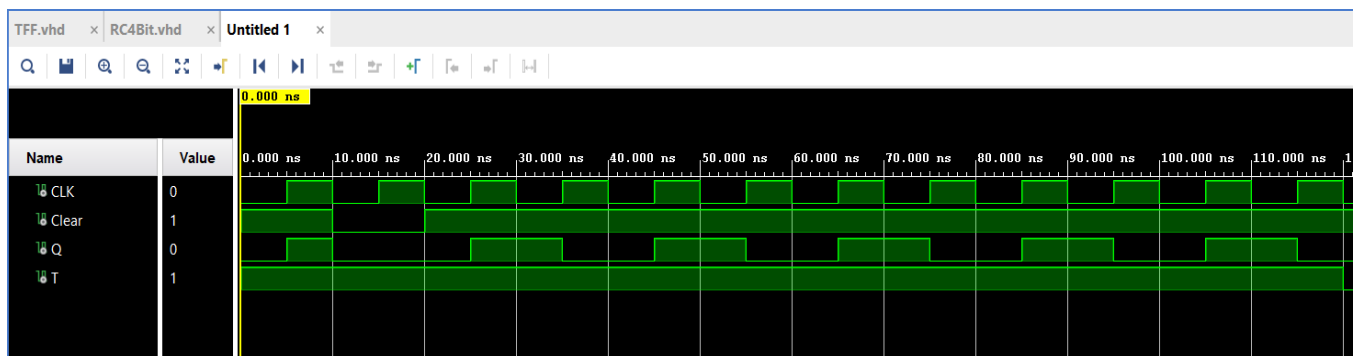


2- 4-bit Asynchronous Counter :

I had Designed a 4-bit asynchronous ripple counter using the previous T flip-flop as a component.

My counter ports:

 - CLK.**
- Enable:** Active High Enable.
- Reset:** Active Low Reset.
- Q:** (4-bit output).



4-bit Asynchronous Counter VHDL CODE :


```

TFF.vhd x RC4Bit.vhd x Untitled 1 x
E:/projects/EX3_4BRC_Part1/EX3_4BRC.srcs/sources_1/new/RC4Bit.vhd

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity RC4Bit is
4     Port ( CLK : in STD_LOGIC;
5           E : in STD_LOGIC;
6           R : in STD_LOGIC;
7           Q : out STD_LOGIC_VECTOR (3 downto 0));
8 end RC4Bit;
9 architecture Behavioral of RC4Bit is
10 component TFF port (
11     T : in STD_LOGIC;
12     CLK : in STD_LOGIC;
13     Clear : in STD_LOGIC;
14     Q : out STD_LOGIC;
15     Qbar : out STD_LOGIC
16 );
17 end component;
18 signal Qb:std_logic_vector(3 downto 0);
19 begin
20 mod1 : TFF port map(E,CLK,R,Q(0),Qb(0));
21 mod2 : TFF port map(E,Qb(0),R,Q(1),Qb(1));
22 mod3 : TFF port map(E,Qb(1),R,Q(2),Qb(2));
23 mod4 : TFF port map(E,Qb(2),R,Q(3),Qb(3));
24 end Behavioral;


```

4-bit Asynchronous Counter simulation :

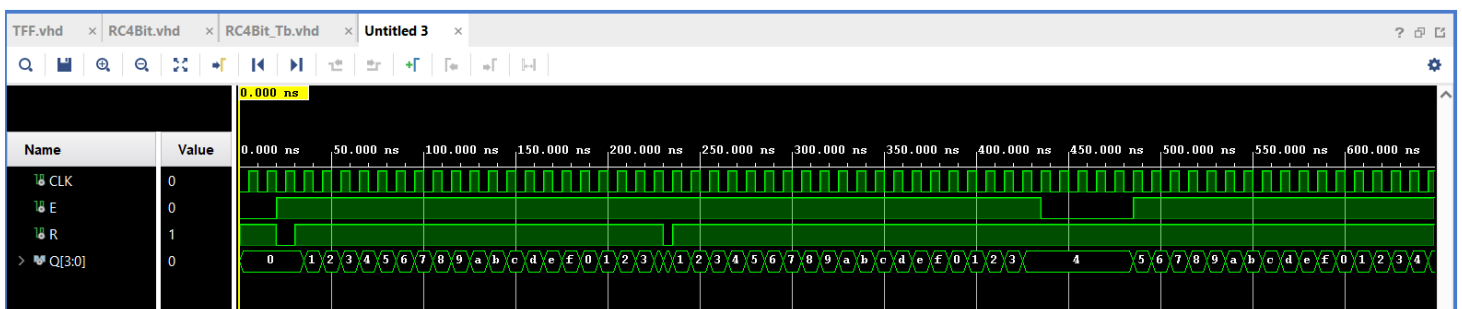

3- Clock Divider :

 Because the system is operating on 100MHz frequency, I completed clock divider to generate an output clock with 1Hz frequency.




Clock Divider VHDL CODE :

E:/projects/EX3_4BRC_Part1/EX3_4BRC.srcs/sources_1/new/Divider.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.std_logic_unsigned.all;
4 use IEEE.numeric_std.ALL;
5 entity Divider is
6     Port ( CLK_IN : in STD_LOGIC;
7           CLK_OUT : out STD_LOGIC);
8 end Divider;
9
10 architecture Behavioral of Divider is
11     signal count:integer range 0 to 50000000:=0;
12     signal CLK : std_logic := '0';
13 begin
14     process (CLK_IN)
15     begin
16         if (CLK_IN'event and CLK_IN='1') then
17             if (count=50000000) then
18                 CLK<=not CLK;
19                 count<=0;
20             else
21                 count<= count +1;
22             end if;
23         end if;
24     end process;
25     CLK_OUT <= CLK;
26 end Behavioral;
27
```

4- Top-Level Entity:

 
The top level entity include two component : clock divider & asynchronous counter as shown in the figure.



Top-Level Entity VHDL CODE:

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity TLEofDand4BRC is
4     Port ( CLK : in STD_LOGIC;
5           E : in STD_LOGIC;
6           R : in STD_LOGIC;
7           Q : out STD_LOGIC_VECTOR (3 downto 0));
8 end TLEofDand4BRC;
9
10 architecture Behavioral of TLEofDand4BRC is
11     component RC4Bit port (
12         CLK : in STD_LOGIC;
13         E : in STD_LOGIC;
14         R : in STD_LOGIC;
15         Q : out STD_LOGIC_VECTOR (3 downto 0)
16     );
17 end component;
18 component Divider port (
19     CLK_IN : in STD_LOGIC;
20     CLK_OUT : out STD_LOGIC
21 );
22 end component;
23 signal CLKto:std_logic;
24 begin
25     Divmod:Divider port map (
26         CLK_IN=>CLK,
27         CLK_OUT=>CLKto
28     );
29     RC4Bitmod:RC4Bit port map (CLKto,E,R,Q);
30 end Behavioral;
31
```

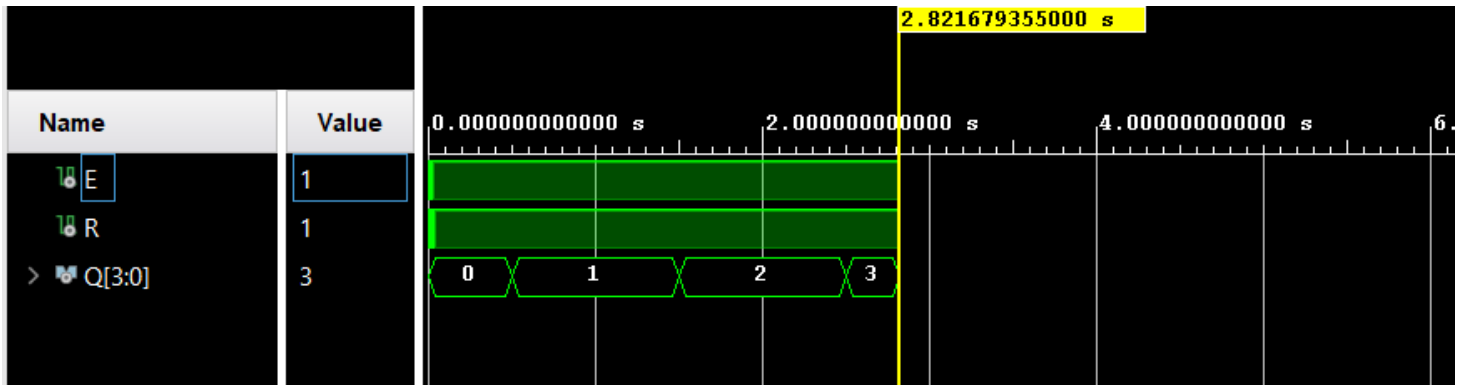Top-Level Entity asynchronous counter Simulation:



This is not the full simulation because it's hard to simulate real time in personal PC

5- Synthesis, Implementation, and Bitstream Generation:

I connected the pins as shown and tested the circuit .

- Reset: SW0
- Enable: SW1
- CLK: Y9
- Q (4bits): LD3, LD2, LD1, LD0.

Inputs	Package Pin	I/O Std
SW0	F22	LVC MOS18
SW1	G22	LVC MOS18
CLK	Y9	LVC MOS33
Outputs	Package Pin	I/O Std
LD0	T22	LVC MOS33
LD1	T21	LVC MOS33
LD2	U22	LVC MOS33
LD3	U21	LVC MOS33

Part 2 : Auto Up Down Synchronous Counter.


The top level entity for Auto Up Down Counter contain two component : divider & Auto Up Down Counter(when UpDown pin is 1 will count rise way and otherwise will count down)

I implemented auto up down counter using VHDL with beaver discretion as shown:


```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.std_logic_unsigned.ALL;
4  entity AutoUpDownCounter is
5      Port (
6          UpDown : in STD_LOGIC;
7          reset : in STD_LOGIC;
8          clk : in STD_LOGIC;
9          cnt : out STD_LOGIC_VECTOR(3 downto 0)
10     );
11 end AutoUpDownCounter;
12 architecture Behavioral of AutoUpDownCounter is
13     signal temp:std_logic_vector(3 downto 0):="0000";
14     begin
15     process (clk,reset)
16     begin
17         if (reset ='0') then
18             temp <= "0000";
19         elsif (clk'event and clk='1') then
20             if (UpDown = '1') then
21                 temp <= temp + '1';
22             else
23                 temp <= temp - '1';
24             end if;
25         end if;
26         cnt <= temp;
27     end process;
28 end Behavioral;

```

 

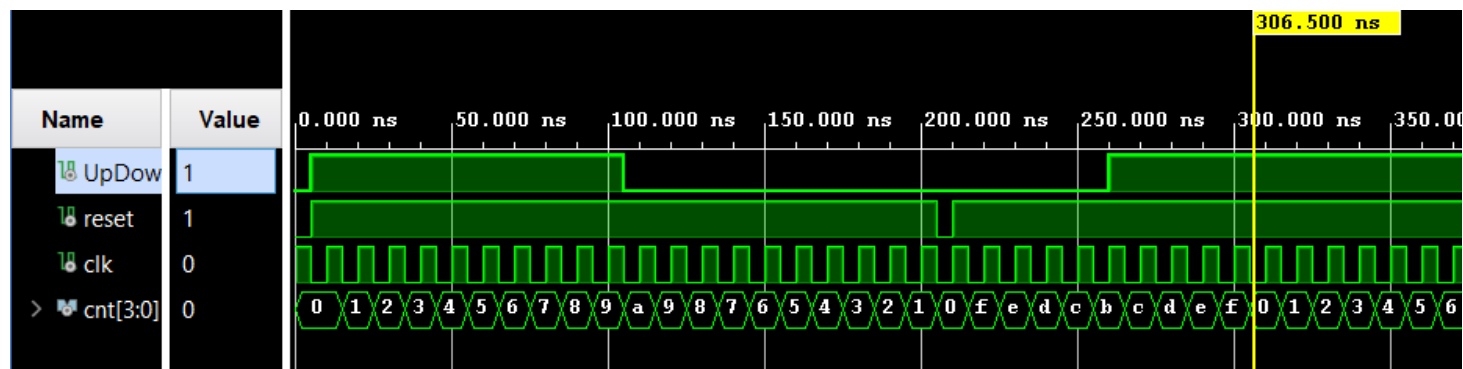And used the same divider in the part 1 .
 Auto Up Down Synchronous Counter Simulation:



Synthesis, Implementation, and Bitstream Generation:

I connected the pins as shown and tested the circuit .

- Reset:** SW0
- UpDown:** SW1
- CLK:** Y9
- Q (4bits):** LD3, LD2, LD1, LD0.

Inputs	Package Pin	I/O Std
SW0	F22	LVCMOS18
SW1	G22	LVCMOS18
CLK	Y9	LVCMOS33
Outputs	Package Pin	I/O Std
LD0	T22	LVCMOS33
LD1	T21	LVCMOS33
LD2	U22	LVCMOS33
LD3	U21	LVCMOS33

Part 3: Push Button UpDown Counter.

In this part I used the same counter in the previous part (part 2).and instead of using direct clock I used a Push Button .as a result new problem Appeared (noise in the Push Button)so the counter will count several times when I push the button. we can fix it easily with Push Button Debouncer algorithm.

A- Build Debouncer Block :

When the Debouncer detect noise
 It move to wait state for 10 ms
 And then output the result.




Debouncer VHDL CODE:

```


11 architecture Behavioral of PBDebouncer is
12   constant COUNT_MAX:integer := 1000000;
13   SIGNAL BTN_ACTIVE : std_logic := '0';
14   signal count : integer := 0;
15   type state_type is (idle,wait_time);
16   signal state : state_type := idle;
17   begin
18   process (CLK)
19   begin
20     if (CLK'event and CLK='1') then
21       case (state) is
22         when idle =>
23           if (PB /= BTN_ACTIVE) then
24             state <= wait_time;
25           else
26             state <= idle;
27           end if;
28         when wait_time =>
29           if (count = COUNT_MAX) then
30             count <= 0;
31             BTN_ACTIVE <= NOT BTN_ACTIVE;
32             state <= idle;
33           else
34             count <= count + 1;
35           end if;
36         end case;
37       end if;
38     end process;
39     PB_debounced <= BTN_ACTIVE;
40   end Behavioral;

```

Debouncer Simulation :

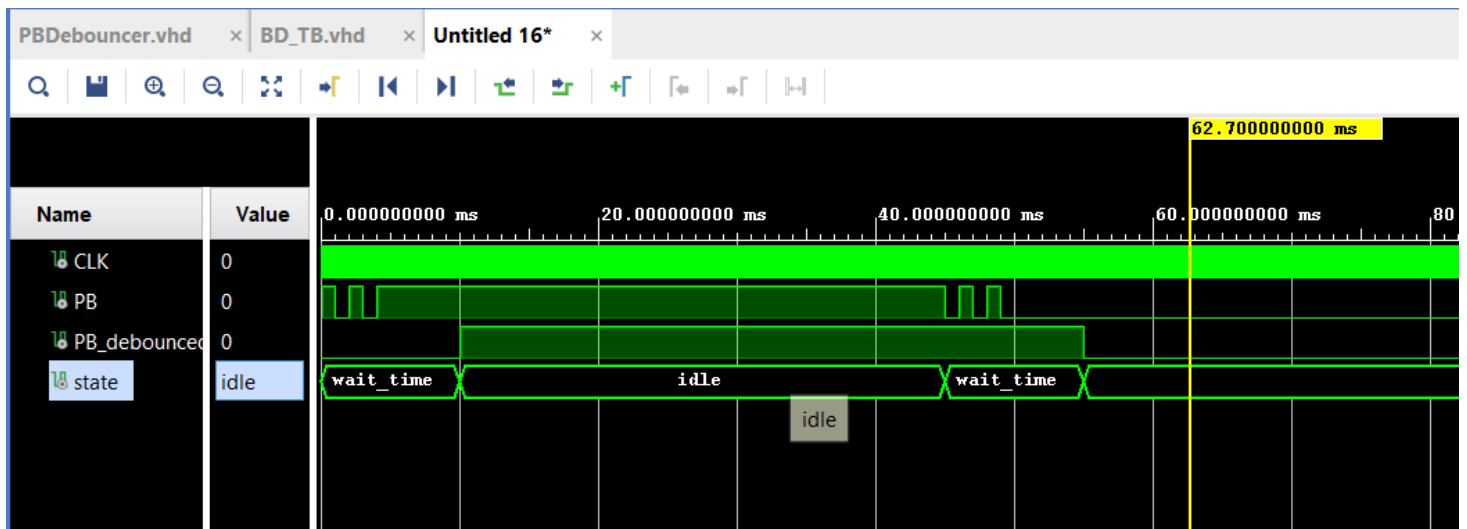

B- Top level Push Button UpDown Counter:

 

VHDL CODE :

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  entity PBUpDownCounter is
4      Port (
5          CLK : in STD_LOGIC;
6          Reset : in STD_LOGIC;
7          UpDown : in STD_LOGIC;
8          PB : in STD_LOGIC;
9          cnt : out STD_LOGIC_VECTOR (3 downto 0)
10     );
11 end PBUpDownCounter;
12 architecture Behavioral of PBUpDownCounter is
13     component AutoUpDownCounter Port (
14         UpDown : in STD_LOGIC;
15         reset : in STD_LOGIC;
16         clk : in STD_LOGIC;
17         cnt : out STD_LOGIC_VECTOR(3 downto 0)
18     );
19 end component;
20 component PBDebouncer Port (
21     CLK : in STD_LOGIC;
22     PB : in STD_LOGIC;
23     PB_debounced: out STD_LOGIC
24 );
25 end component;
26 signal PB_debounced2:std_logic;
27 begin
28     mod1 : PBDebouncer port map(CLK,PB,PB_debounced2);
29     mod2 : AutoUpDownCounter port map (UpDown,reset,PB_debounced2,cnt);
30 end Behavioral;
```


Synthesis, Implementation, and Bitstream Generation:

I connected the pins as shown and tested the circuit .

	Signal Name	Package Pin	I/O Std
Up Button	BTNU	T18	LVCMOS18
Right Button	BTNR	R18	LVCMOS18
Down Button	BTND	R16	LVCMOS18
Center Button	BTNC	P16	LVCMOS18
Left Button	BTNL	N15	LVCMOS18

 
Part 4: Two-Digit BCD Counter.

In this part, I built a two-digit BCD counter that counts from 00 to 99. And the result displayed on a two-seven-segment display common cathode module connected to the kit. The circuit diagram for this module is shown in Fig1.



The circuit contain four blocks :

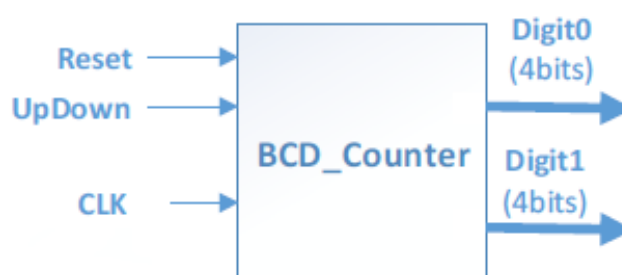- 1- Divider : the same as the Divider in Part 2
- 2- BCD_Counter: It is a two-digit (two-decade) BCD counter counts in decimal from 00 decimal to 99.




```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use ieee.numeric_std.all;
4  use ieee.std_logic_unsigned.all;
5  entity BCD_Counter is
6  Port (
7      clk : in STD_LOGIC;
8      Reset : in STD_LOGIC;
9      UpDown: in STD_LOGIC;
10     Digit0: out STD_LOGIC_VECTOR (3 downto 0);
11     Digit1: out STD_LOGIC_VECTOR (3 downto 0));
12 end BCD_Counter;
13 architecture Behavioral of BCD_Counter is
14
15     signal temp0,temp1:std_logic_vector(3 downto 0):="0000";
16
17 begin
18     process (clk,Reset,UpDown)
19     begin
20         if (Reset = '0') then
21             temp0<="0000";
22             temp1<="0000";
23         else
24             if (clk'event and clk='1')then
25                 if (UpDown='1')then
26                     if (temp0 < "1001")then
27                         temp0<=temp0+'1';
28                     else
29                         temp0<="0000";
30                     if (temp1<"1001")then
31                         temp1<=temp1+'1';
32

```

```


32
33         else
34             temp1<="0000";
35         end if;
36     end if;
37     elsif (UpDown='0') then
38         if (temp0 > "0000") then
39             temp0<=temp0-'1';
40         else
41             temp0<="1001";
42             if (temp1>"0000") then
43                 temp1<=temp1-'1';
44             else
45                 temp1<="1001";
46             end if;
47         end if;
48     end if;
49     else
50         null;
51     end if;--2
52 end if;--1
53 Digit0<=temp0;
54 Digit1<=temp1;
55 end process;
56 end Behavioral;

```

The timing diagram displays the behavior of the BCD counter over 600,000 ns. The signals shown are:

- clk**: A periodic clock signal.
- Reset**: A signal that is active low, remaining low for the first 100,000 ns and then high.
- UpDown**: A signal that is active low, remaining low for the first 200,000 ns and then high.
- Digit0[3:0]**: A 4-bit output showing hexadecimal values. It starts at 0, increments to 9 at 100,000 ns, decrements to 0 at 200,000 ns, and continues to cycle between 0 and 9.
- Digit1[3:0]**: A 4-bit output showing hexadecimal values. It starts at 0, increments to 1 at 100,000 ns, decrements to 0 at 200,000 ns, and continues to cycle between 0 and 9.

 To continuously display a digit on each display faster than the human eye (10 ms) can respond .so the time-mux will change the digit to display it .



```


architecture Behavioral of Time_MUX is
    signal count:integer range 0 to 1000000:=0;
    signal CLK1 : std_logic := '0';
begin
    process(clk)
    begin
        if (clk'event and clk='1') then
            if (count=1000000) then
                CLK1<=not CLK1;
                count<=0;

            else
                count<= count +1;
            end if;
        end if;
        if (CLK1='0') then
            BCD_Value<=Digit0;
        else
            BCD_Value<=Digit1;
        end if;
    end process;

    DigSelect <= CLK1;
end Behavioral;


```

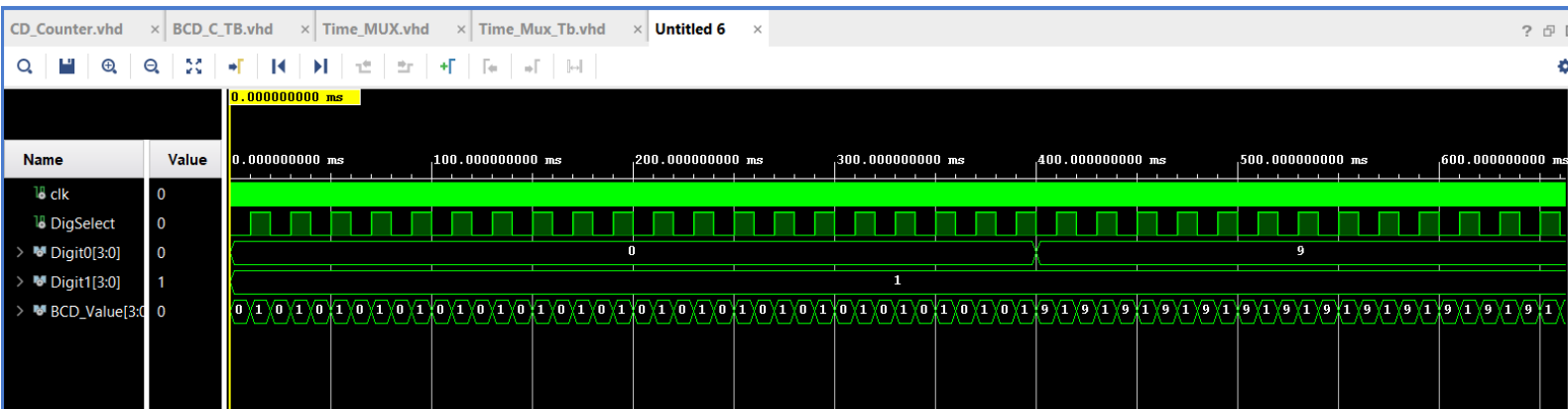Time_MUX simulation :
Assume two bcd digit (10) and (19)




4- BCD_To_SevenSeg:

 To decode the binary value and prepped it to display



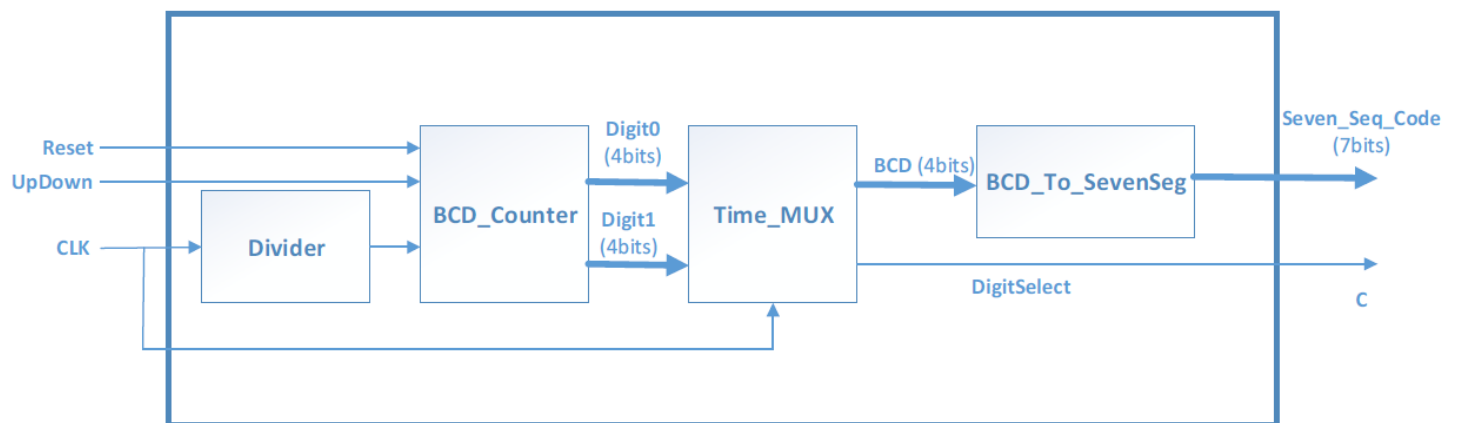And finally we got the top level component of Two-Digit BCD Counter:



Synthesis, Implementation, and Bitstream Generation:

I connected the pins as shown and tested the circuit .

Inputs	Package Pin	I/O Std
Reset => SW0	F22	LVC MOS18
SW1	G22	LVC MOS18
CLK	Y9	LVC MOS33

Signal Name	Package Pin	I/O Std
JA1	Y11	LVC MOS33
JA2	AA11	LVC MOS33
JA3	Y10	LVC MOS33
JA4	AA9	LVC MOS33
JB1	W12	LVC MOS33
JB2	W11	LVC MOS33
JB3	V10	LVC MOS33
JB4	W8	LVC MOS33

Dig select =>

Conclusion:

In this experiment I learned how to build 4 bit ripple counter using T-Flip flops , how to build Auto Up Down Synchronous Counter (behavior), how to Debounce a Push Button ,and i become familiar with Two-Digit BCD Counter.